

Analogue Design

A Proportional to Temperature Current Source (PTAT) Tutorial Kevin Aylward B.Sc.

[Back to Contents](#)

Overview

This tutorial describes the essentials of the design of a Proportional To Absolute Temperature (PTAT) current source.


A PTAT current generator is an inherent core topology in the design of “Bandgap” voltage references. Typically, a positive slope with temperature PTAT current is passed through a resistor to generate a PTAT voltage that is added to a negative with temperature slope PTAT voltage. The negative slope PTAT usually being the V_{be} of a diode, or diode connected transistor. This summed voltage is so arranged so that the individual PTAT cancel each other and result in a nominally zero variation of voltage with temperature output voltage.

Delta V_{be} Source

The starting point of the PTAT generator is a topology referred to as a delta- V_{be} current source.


Consider the following circuit with a voltage source, V_{IN} , swept from 0v to some final voltage:

Fig. 1

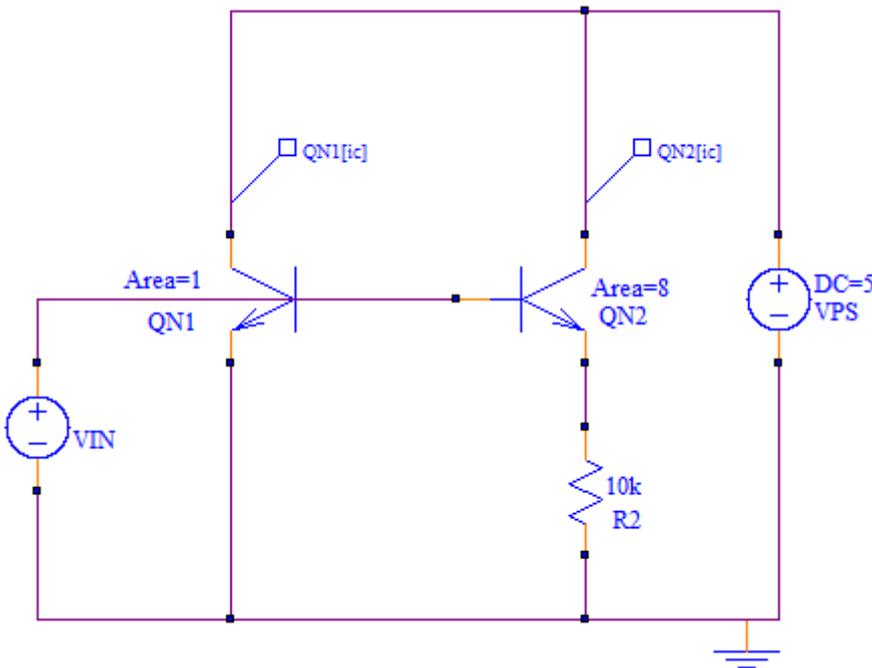

For small V_{IN} voltages, the currents are low, such that there is a negligible voltage drop across R_2 . Q_{N2} is chosen to have a much larger area than Q_{N1} , so Q_{N2} 's current will be larger than the current of Q_{N1} , and initially increase exponentially at a much faster rate than the current of Q_{N1} as V_{IN} is increased. However, in the limit of large V_{BE} voltages, R_2 will limit Q_{N2} 's current to the order of V_{IN} less than about 0.7V divided by R_2 . In contrast, the current of Q_{N1} , will keep increasing exponentially. This results in the following type of graphs for the currents of Q_{N1} and Q_{N2} .

Fig. 2

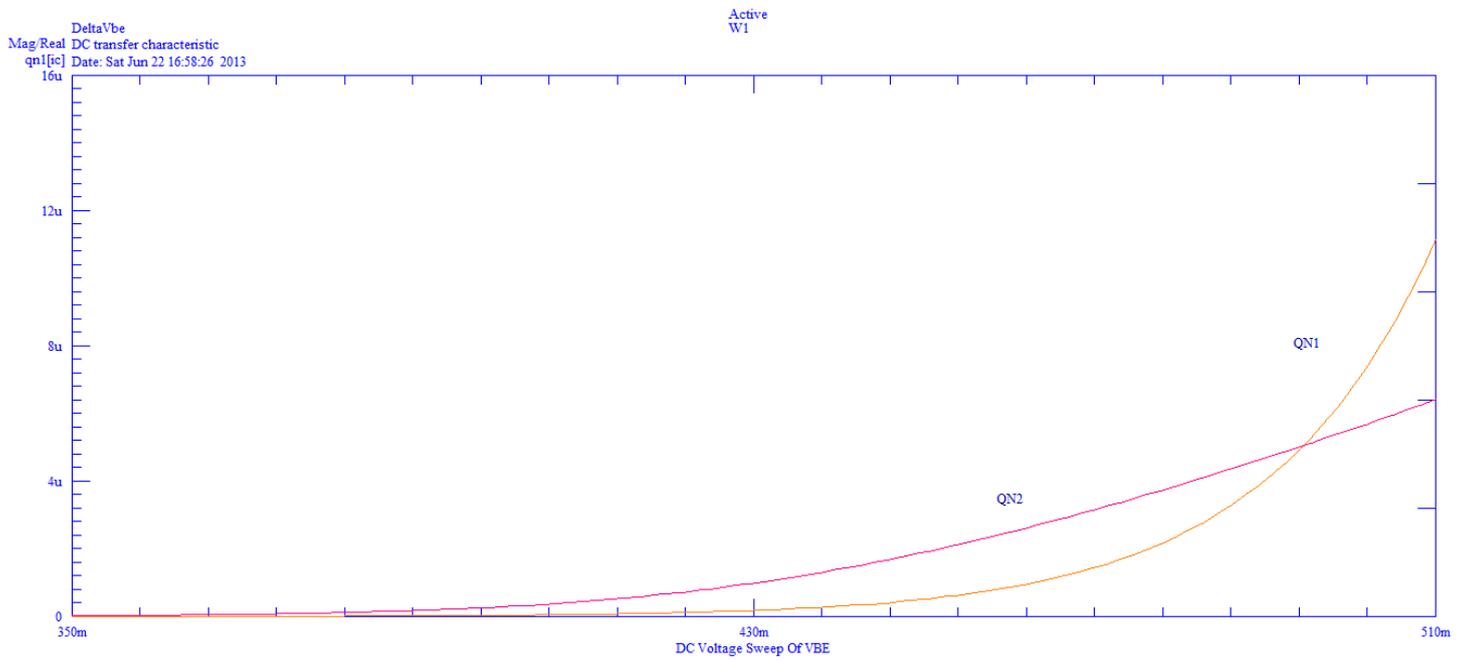

It can be seen from the graph, that there is an intersection of the currents of QN1 and QN2. That is, there are two points where the currents of QN1 and QN2 are equal. One point is at zero V_{IN} , being zero current in both transistors, the second point being at a “special” equality point.

Operating Point v Temperature

The collector/emitter current in a transistor can be shown to be related to its base emitter voltage as:

$$I_c = I_s(T)(e^{\frac{V_{be}}{V_t}} - 1)$$

$$\text{where } V_t = \frac{q}{KT}$$

Or, neglecting the 1 for $V_{be} \gg 0$:

$$I_c = I_s(T)e^{\frac{V_{be}}{V_t}}$$

From inspection of the schematic Fig. 1, the currents in QN1 and QN2 can therefore be expressed as:

$$I_{cqn1} = I_s e^{\frac{V_{in}}{V_t}}, I_{cqn2} = A_r I_s e^{\frac{V_{in} - I_{cqn2}R}{V_t}}$$

$$I_{cqn1} = \frac{I_{cqn2}}{A_r} e^{\frac{I_{cqn2}R}{V_t}} \text{ and see for example, [Widlar Current Source](#)}$$

A_r being the relative ratio of transistor emitter areas.

At the stable intersection point, the currents are equal such that:


$$A_r = e^{\frac{I_{cqn2}R}{V_t}}$$

$$I_{cqn2} = \frac{V_t}{R} \ln(A_r) = \frac{\Delta V_{be}}{R}$$

$$I_{cqn2} = \frac{KT}{Rq} \ln(A_r)$$

Thus, there is a linearly increasing current in QN1 and QN2 with respect to temperature. This current is referred to as a PTAT current.

Fig. 4

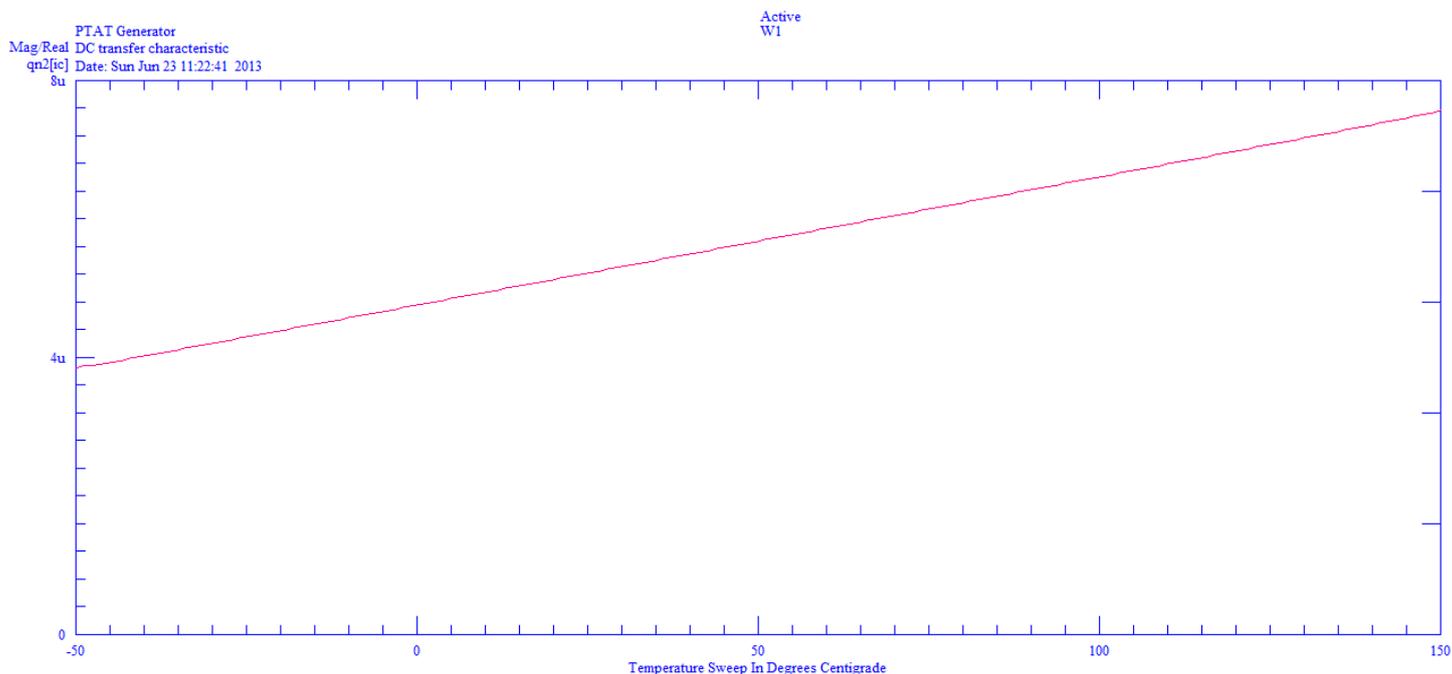

Start-up Design Procedure

The start-up circuit needs to reliably start the PTAT loop yet turn off once the PTAT loop is started. In general, this is a straightforward procedure with modern design simulation tools. However, it should be appreciated that, in principle, as there is more than one numerical solution to the equations of the circuit, [SPICE](#) might well find the one you want without the start-up circuit actually being responsible. That is, the start-up circuit might be faulty, but it is not apparent from the simulations! Fortunately, the simulation results themselves can be used to effectively prove that the start-up circuit must work.

The basic principals are:

- A Ensure that the minimum current in QN1, over all operating conditions in its valid loop state, will force enough current in MP4 to fully turn off MP3.
- B That the start-up generates enough current to force the PTAT loop to start. That is, overcomes potential losses such as very low current gain at low currents.
- C Leakages (e.g. at high temperatures) do not keep the start-up circuit either on (MP3) when it should be off, or off (MP4) when it should be on.
- D **NEVER** use start-up circuits that are dynamic (e.g. caps) or relies on leakages (e.g. diodes).

There are many ways to implement a start-up circuit. The method used here is just an example. Some may be easier to check for reliability, but may have other blemishes.

Design

Determine the minimum $I_{qn2} \sim \frac{\Delta V_{be}}{R_{max}}$


Determine the maximum $I_{startup} \sim \frac{VPS_{max}}{R_{min}}$


Tests

- 1 Run VPS DC and Slow VPS TRAN sweeps over all process corners and temperatures.
- 2 Run Temperature sweeps over all process corners and DC VPS values.
- 3 Check minimum current of QN1 multiplied by its transfer ratio to MP4 sinks the max current of RSTARTUP by a factor of two to four. This will guarantee that MP3 is off when the bandgap is started. This ratio is kept large enough, but not so large that MP3 is always shunted off by MP4 leakage and otherwise fail to start bandgap.
- 4 Check that the leakage from MP3 is minimal.
- 5 Check that there are no start-up limit cycle oscillations of the start-up loop on transient power ups (rare), compensate if required. A capacitor to supply/ground at the resistor node is usually sufficient.
- 7 To check.

Set RCHECK to a very high value. Run the above corners again. MP3 now forms a negative feedback loop and will now set the V_{be} voltage node. Check that the max current in QN1 is always less than its minimum when QN1 is connected normally. This proves that the start-up loop cannot force a third stable state. The check here is to ensure that the start-up loop can not hold the circuit at a higher current than that set by the PTAT loop. The PTAT loop will still force this current to go higher when re-connected, and by the above, shut off QP3.

Sample WC Process Corner Runs

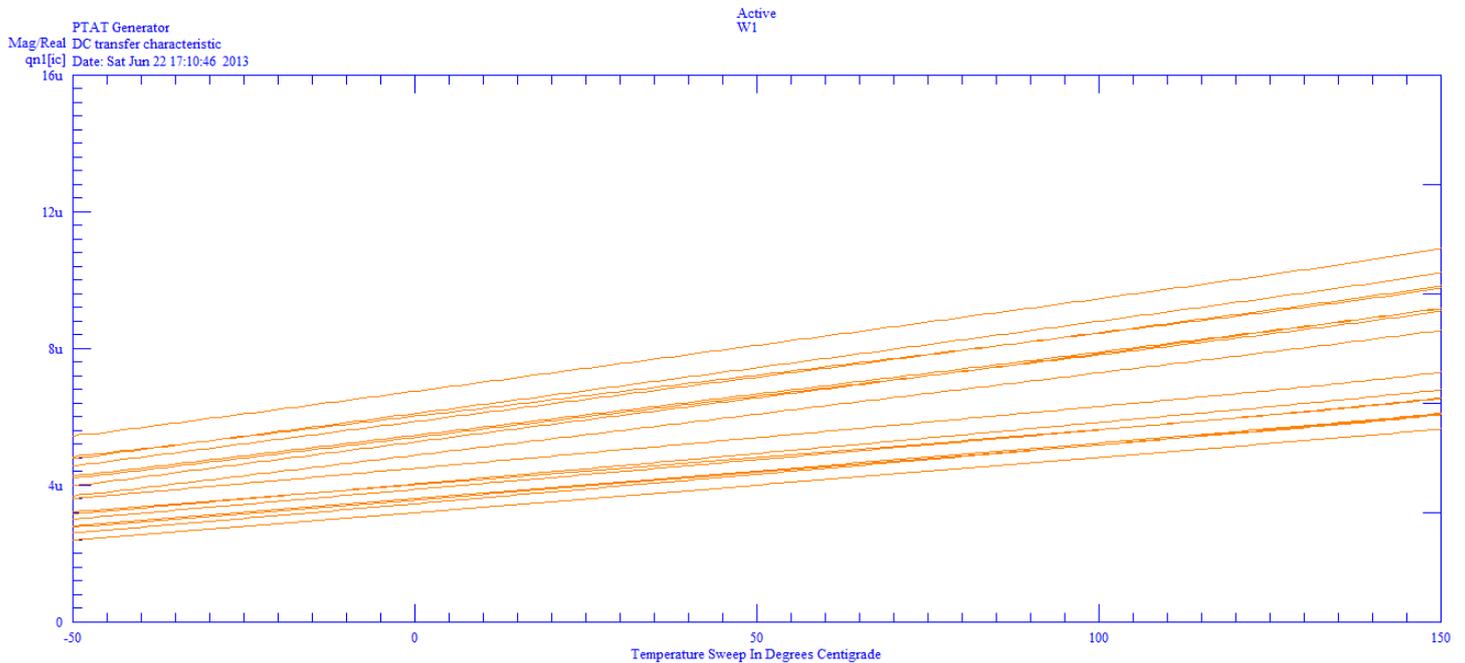

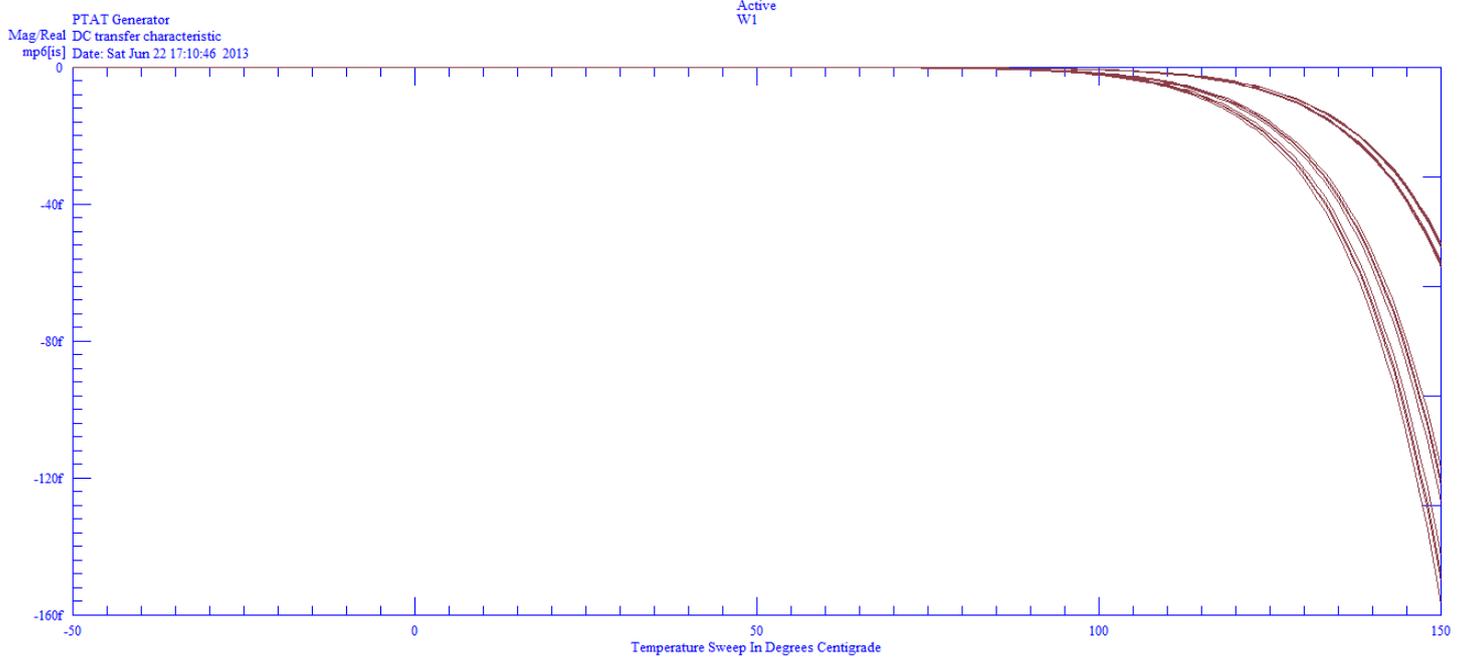

© Kevin Aylward 2013
All rights reserved
providing that this source is acknowledged.
Website last modified 23rd June 2013
www.kevinaylward.co.uk
